

**LAB # 10**  
**Active Filters**



**SUBMITTED BY:**

Awais Saddiqui

**REG NO:**

21PWCSE1993

**SECTION:**

“A”

**SUMITTED TO:**

Engineer Faiz Ullah Sir

**UNIVERSITY OF ENGINEERING AND TECHNOLOGY PESHAWAR**  
**COMPUTER SYSTEM ENGINEERING**

## ASSESSMENT RUBRICS

LAB REPORT ASSESSMENT				
Criteria	Excellent	Average	Nil	Marks Obtained
1. Objectives of Lab	All objectives of lab are properly covered [Marks 1]	Objectives of lab are partially covered [Marks 0.5]	Objectives of lab are not shown [Marks 0]	
2. Procedure	All experimental steps are shown. [Marks 2]	Some of the experimental steps are shown. [Marks 1]	Experimental steps not shown [Marks 0]	
3. Demonstration of Concepts	The student demonstrated a clear understanding of the assignment concepts [Marks 2]	The student demonstrated a clear understanding of some of the assignment concepts [Marks 1]	The student failed to demonstrate a clear understanding of the assignment concepts [Marks 0]	
4. Experimental Results	All experimental results are completely shown in form of table [Marks 3]	Experimental results are partially shown and some of the observations are missing [Marks 1.5]	No experimental results are shown [Marks 0]	
5. conclusion	Conclusion of the lab is properly written [Marks 2]	Conclusion of the lab is partially written [Marks 1]	Conclusion of lab is not written [Marks 0]	
<p style="text-align: right;">Total Marks Obtained: _____</p> <p style="text-align: center;">Instructor Signature: _____</p>				

## Low Pass Filter

### Objectives:

To study the Active Low pass filter and to evaluate:

- High cutoff frequency of Low pass filter.
- Pass band gain of Low pass filter.
- Plot the frequency response of Low pass filter.

### Equipment:

1. DC power supplies +15V, -15V from external source
2. Function generator
3. Oscilloscope
4. Digital Multimeter

### Components:

1. Resistance 10k $\Omega$
2. Resistance 22k $\Omega$
3. Capacitor 0.01 $\mu$ F
4. LM 741

### Equation of low pass filter

$V_{in}$  = Input signal Voltage

$V_{out}$  = Output signal Voltage

$|V_{out}/V_{in}|$  = Gain of filter as a function of frequency

$AF = 1 + R_F/R_1$  = pass band gain of filter

$f$  = frequency of input signal

$f_H = 1/2\pi RC$  = high cut off frequency, 3-dB frequency, corner frequency

Operation of low pass filter using equation 2

The ideal low pass filter has a constant gain AF from 0 to high cut off frequency ( $f_H$ ) at  $f_H$  the gain is  $0.707 * AF$ , and after  $f_H$  it decreases at a constant rate with an increase in frequency i.e., when input frequency is increased tenfold (one decade), the voltage gain is divided by 10. Gain (dB) =  $20 \log |V_{out} / V_{in}|$  i.e., Gain Roll off rate is  $-20\text{dB} / \text{decade}$ .

## Procedure

1. Connect the circuit as shown in Figure 2.
2. Switch ON the power supply
3. Connect a sinusoidal signal of amplitude 1V (p-p) of frequency 1KHz to  $V_{in}$  of Low pass filter from function generator
4. Connect Ch-1 of oscilloscope to the signal source
5. Observe output on Ch-2 of oscilloscope
6. Increase the frequency of input signal step by step and observe the effect on output  $V_{out}$  on oscilloscope
7. Tabulate values of  $V_{out}$ , gain, gain (dB) at different values of input frequency shown in observation Table 2.
8. Plot the frequency response of low pass filter using the data obtained at different input frequencies.

## Theoretical Calculations:


Calculate all the following values

1. Pass band gain of Low pass filter  $AF = 1 + R_F / R_1$
2. Pass band gain (dB) =  $20 \log |V_{out} / V_{in}|$
3. 3 dB frequency  $f_H = 1/2\pi RC$

4. Gain at 3 dB frequency  $f_H = 0.707 * A_F$

5. Roll off rate =  $-20\text{db/decade}$

## Proteus Circuit:

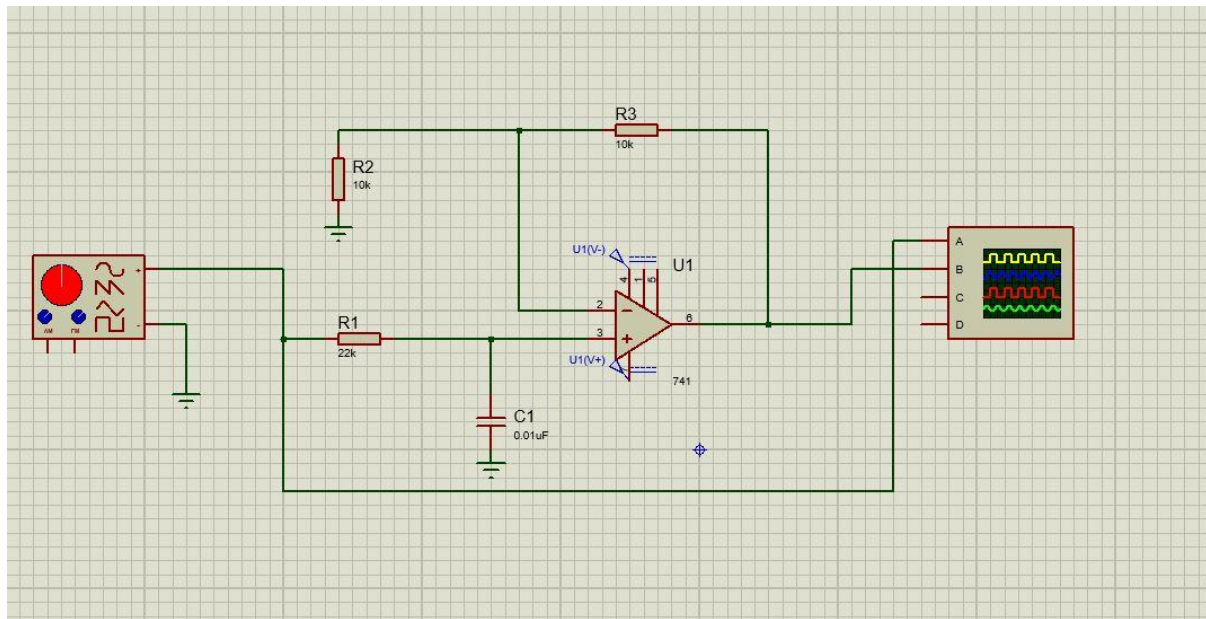

## Results:

	Theoretical	Practical
Pass band gain ( $A_r$ )	2	2
Pass band gain ( $A_r$ ) in db	6	6
3db frequency $f_H$	723	722
Gain at 3db frequency ( $f_H$ ) in db	1.414	1.414

**Table 2:**

S.No	Input Frequency (Hz)	$V_{out}$	$ V_{out}/V_{in}  = \text{Gain}$	$\text{Gain}(\text{db}) = 20\log  V_{out}/V_{in} $
1	300	9.18	1.8	5.182
2	500	8.2	1.62	4.1

3	700	7.33	1.44	3.3
4	1k	5.79	1.15	1.5
5	5k	1.43	0.28	-11.4
6	10k	0.70	0.14	-16.8
7	15k	0.4	0.096	-20.33

## Conclusion:

A low-pass filter is a filter that passes signals with a frequency lower than a selected cutoff frequency and attenuates signals with frequencies higher than the cutoff frequency. The exact frequency response of the filter depends on the filter design.